

CS 211: Computer Architecture

Programming Assignment 4: Circuit Simulator

Introduction

You have to write a circuit simulator. One of the inputs to your program will be a circuit description file that will describe a circuit using various directives. Your program will print the output of the circuit for all possible input values.

1 Circuit Description Directives

The input variables used in the circuit are provided using the `INPUTVAR` directive. The `INPUTVAR` directive is followed by the number of input variables and the names of the input variables. All the input variables will be named with capitalized identifiers. An identifier consists of at least one character (A-Z) followed by a series of zero or many characters (A-Z) or digits (0-9). For example, some identifiers are `IN1`, `IN2`, and `IN3`. An example specification of the inputs for a circuit with three input variables: `IN1`, `IN2`, `IN3` is as follows:

```
INPUTVAR 3 IN1 IN2 IN3
```

The outputs produced by the circuit is specified using the `OUTPUTVAR` directive. The `OUTPUTVAR` directive is followed by the number of outputs and the names of the outputs.

An example specification of the circuit with output `OUT1` is as follows:

```
OUTPUTVAR 1 OUT1
```

The circuits used in this assignment will be built using the following building blocks: `NOT`, `AND`, `OR`, `NAND`, `NOR`, and `XOR`.

The building blocks can produce temporary variables as outputs. Further, these building blocks can use either the input variables, temporary variables, a boolean '1' or a '0' as input.

Note: Output variables will never be used as inputs in a building block.

All the temporary variables will also be named with lower case identifiers (i.e., `temp1`, `temp2`, `temp3`, ...).

The specification of each building block is as follows:

- `NOT`: for example,

```
NOT IN1 OUT1
```

- `AND`: for example,

```
AND IN1 IN2 OUT1
```

- `OR`: for example,

```
OR IN1 IN2 OUT1
```

- `NAND`: for example,

```
NAND IN1 IN2 OUT1
```

- NOR: for example,

```
NOR IN1 IN2 OUT1
```

- XOR: for example,

```
XOR IN1 IN2 OUT1
```

2 Describing Circuits using the Directives

It is possible to describe any combinational circuit using the above set of directives. For example, the circuit $OUT1 = IN1.IN2 + IN1.IN3$ can be described as follows:

```
INPUTVAR 3 IN1 IN2 IN3
OUTPUTVAR 1 OUT1
AND IN1 IN2 temp1
AND IN1 IN3 temp2
OR temp1 temp2 OUT1
```

Note that `OUT1` is the output variable. `IN1`, `IN2`, and `IN3` are input variables. `temp1` and `temp2` are temporary variables.

A circuit description is a sequence of directives. You can assume that every temporary variable occurs as a output variable in the sequence before occurring as an input variable.

Note: A temporary variable can occur as an output variable in at most one directive.

3 Format of the Input Files

Your program will be given one file as input, containing the description of a circuit using the directives described above.

For example:

```
INPUTVAR 3 IN1 IN2 IN3
OUTPUTVAR 1 OUT1
AND IN1 IN2 temp1
AND IN1 IN3 temp2
OR temp1 temp2 OUT1
```

4 The problem

You have to write a program called `first` as described above. You are guaranteed that the circuit descriptions given as input to your program will be sorted. Let's look at an example we have encountered before.

Example Execution

Suppose a circuit description file named `circuit.txt` has the description for the circuit $OUT1 = IN1.IN2 + IN1.IN3$

```
INPUTVAR 3 IN1 IN2 IN3
OUTPUTVAR 1 OUT1
AND IN1 IN2 temp1
AND IN1 IN3 temp2
OR temp1 temp2 OUT1
```

Then, on executing the program with the above circuit description file, your program should produce the following output:

```
./first circuit.txt
0 0 0 0
0 0 1 0
0 1 0 0
0 1 1 0
1 0 0 0
1 0 1 1
1 1 0 1
1 1 1 1
```

The output of the first three columns are `INPUTVAR IN1`, `IN2`, and `IN3` respectively. And the last column denotes the `OUTPUTVAR OUT1`.

Note: the values of the input and output variables should be space separated and be in the same order as the output variables in the `INPUTVAR` and `OUTPUTVAR` directive, e.g., if the circuit description file has the directive `INPUTVAR 3 IN1 IN2 IN3`, and `OUTPUTVAR 3 OUT1 OUT2 OUT3`, then the first values should be those of the input variables `IN1`, `IN2`, and `IN3`, and output variable `OUT1`, followed by that of `OUT2`, and then that of `OUT3`.

5 Submission

Please submit a tar file named `pa4.tar` on Canvas. To create this file, put everything that you are submitting into a directory (folder) named `pa4`. Then, `cd` into the directory containing `pa4` (that is, `pa4`'s parent directory) and run the following command:

```
tar cvf pa4.tar pa4
```

To check that you have correctly created the tar file, you should copy it (`pa4.tar`) into an empty directory and run the following command:

```
tar xvf pa4.tar
```

This should create a directory named `pa4` in the (previously) empty directory.

The `pa4` directory in your tar file must contain one subdirectory. The subdirectory should be named `first` (in lower case). Each directory should contain your source files, header files, and a make file. Running the makefile in the first folder, should produce the binary `first`.

Use the autograder to test your submission during development and before submission as you had done with your other assignments.